

Flying Capacitor Booster

The Advantages and Operation of Flying Capacitor Booster

 


Table of Contents

| | | |
|-------|--|----|
| 1 | Introduction | 5 |
| 2 | The Flying Capacitor Booster | 5 |
| 2.1 | The commutation loops and operation modes of the Flying Capacitor Booster..... | 6 |
| 2.2 | The operation of the Flying Capacitor Booster..... | 9 |
| 2.3 | The advantages of the Flying Capacitor Booster | 11 |
| 3 | The Flying Capacitor..... | 12 |
| 3.1 | Sizing of the Flying Capacitor | 12 |
| 3.2 | The balancing of the capacitor voltage..... | 12 |
| 3.3 | The pre-charge of the capacitor [2]..... | 13 |
| 3.3.1 | Design considerations | 16 |
| 3.3.2 | Patent sublicensing | 17 |
| 4 | Conclusion | 18 |
| 5 | References..... | 18 |



Vincotech

Table of Contents

Revision History

| Date | Revision Level | Description | Page Number(s) |
|-------------|-----------------------|---|-----------------------|
| 01.07.2020 | 1 | First version | 17 |
| 01.06.2022 | 2 | Patent sublicensing section added (chapter 3.3.2) | 17 |

Disclaimer:

The information in this document is given as an indication for the purpose of implementation only and shall not be regarded as any description or warranty of a certain functionality, condition or quality. The statements contained herein, including any recommendation, suggestion or methodology, are to be verified by the user before implementation, as operating conditions and environmental factors may vary. It shall be the sole responsibility of the recipient of this document to verify any function described herein in the given practical application. Vincotech GmbH hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of noninfringement of intellectual property rights of any third party) with respect to any and all information given in this document.

1 Introduction

High efficiency solar inverters getting more and more demand in the recent years. But cost-efficient solutions are also desirable. To achieve this, not only the inverter but also the Booster stage have to be low cost and highly efficient. Two and three level Boosters are commonly used in solar inverters. The three level solutions are able to decrease the voltage stress on the semiconductors and the output voltage ripple; therefore, the inductor size can be decreased. Due to three level operation switched voltage level are half of the DC-link voltage low voltage semiconductors can be used which are faster and cheaper. For three level operation an adequate DC-link capacitor (capacitive voltage divider) have to be utilized which can split the two-level DC voltage into three voltage levels. In this case the PWM signal needs to be corrected to ensure the symmetry of the neutral point of the divider. Usually two inductors are used in the input in three level boosters. This document describes the Flying Capacitor Booster solution, which increase the efficiency while still cost efficient without enormous three level DC-link capacitors and with only one choke on the input.

2 The Flying Capacitor Booster

In this topology the additional voltage levels are synthesized by capacitor, so-called flying capacitor.

In three level case the voltage of the flying capacitor is the half of the output voltage. This capacitor can offset the output voltage with $\frac{V_{DC}}{2}$ in positive and negative direction. The three level Flying Capacitor Booster can be seen on Figure 1.

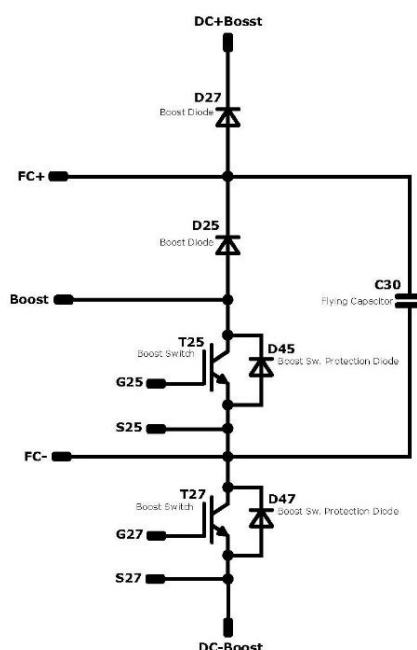


Figure 1 The three level Flying Capacitor Booster

In the flying capacitor booster due to the phase shift (see Chapter 2.2) in the control of transistors the input frequency is p times the switching frequency (p is the number of stages describe later).

2.1 The commutation loops and operation modes of the Flying Capacitor Booster

In Flying Capacitor Booster, the commutation loops are including capacitors. A capacitor from the commutation point of view can be considered zero impedance. It's main role in the commutation loop to offset the two-outer semiconductor from each other. With this offset the three-level flying capacitor booster can be considered as two standalone Booster, where the outer one's commutation loop includes the DC-link capacitor, the outer diode, the flying capacitor and the outer switch. The inner commutation loop includes the flying capacitor, the inner diode and the inner switch. The two commutation loops can be seen on Figure 2.

 


Figure 2 The two commutation loops

In general, the number of voltage levels are theoretically endless, but in practice three, four and five levels are used. The additional levels in n level solution can be realized by adding extra outer commutation loops to the three-level converter. Every added booster's commutation loops will be similar to the blue loop on Figure 2. The number of voltage levels can be calculated as the following:

$$n_{level} = p + 1$$

Where p is number of the commutation loops (boosters). The voltage of the capacitor can be calculated:

$$V_{FC,i} = V_{DC} \cdot \left(1 - \frac{i-1}{p}\right)$$

Where i is number of the given commutation cells. The first loop refers always the most outer loop.

This article will describe the operation and behavior of the three-level flying capacitor booster. All other solution can be realized based on this article.

In the operation of the three-level flying capacitor booster four different mode can be derived. During normal operation the voltage of the flying capacitor is the half of the output voltage and

the inductor current is perpetual. In the first mode all the two switches are off, the current goes thru the two diodes, they are working in bypass mode. In this mode the voltage of the flying capacitor is not changing, the current of the choke is decreasing, the output voltage is increasing. In the second mode, the lower switch (T27) is turned on. The current is charging the flying capacitor resulting its voltage to increase. In the third mode the inner switch is turned on (the outer switch is turned off), the current goes thru the flying capacitor, while its voltage is decreasing, the output voltage will increase. In the last mode, all the two switches are turned on. The voltage of the flying capacitor will be stationary, while the current of the choke will be increasing. In the second and the third mode the inductor current change is depend on the duty cycle (D). The operations and their effects can be seen on Figure 3 and Table 1.

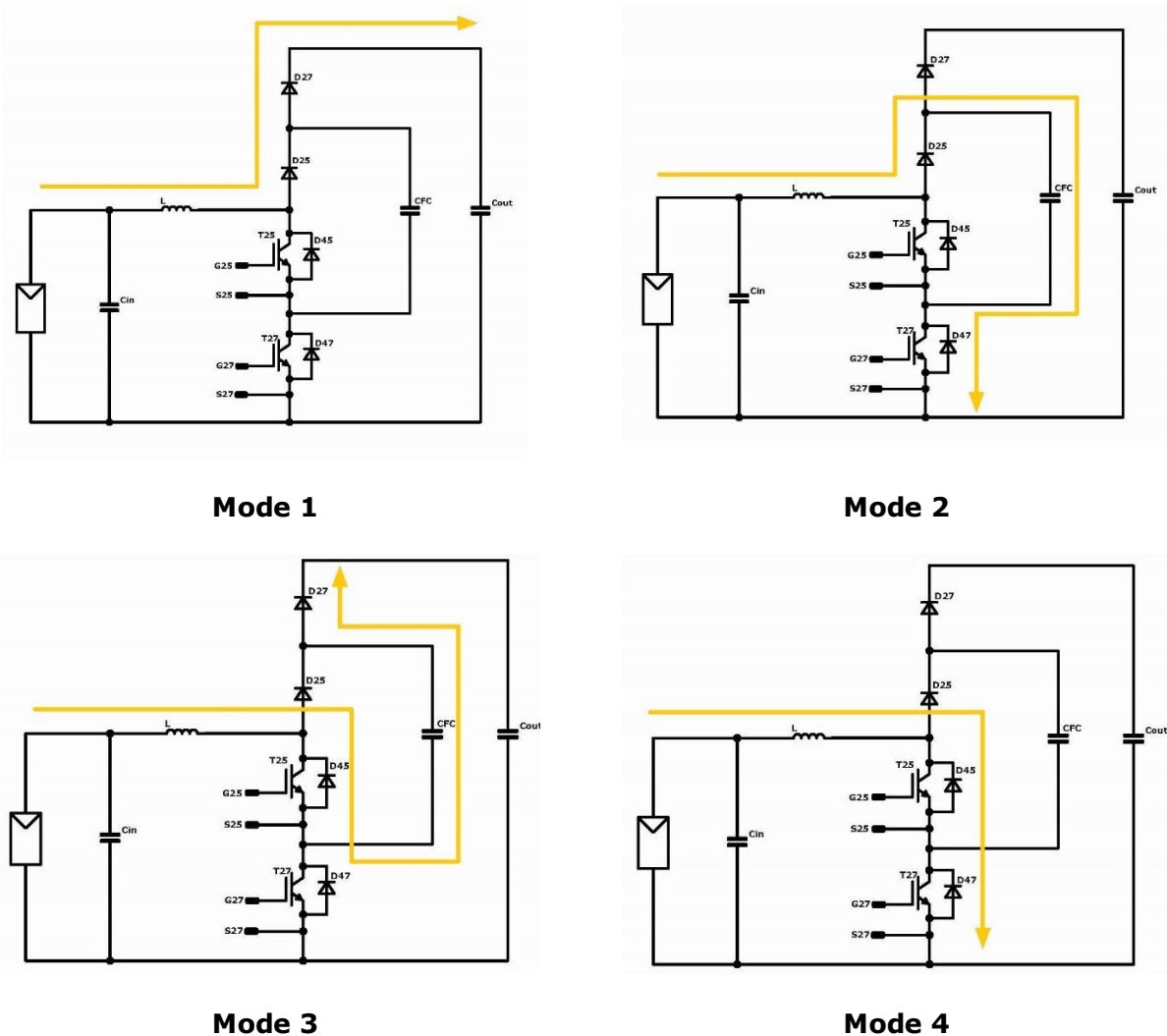


Figure 3 Operation modes of Flying Capacitor Booster

| Mode | Transistors | | Inductor current | | FC voltage | DC-link voltage |
|--------|-------------|-----|------------------|------------|------------|-----------------|
| | T25 | T27 | D<0.5 | D>0.5 | | |
| Mode 1 | OFF | OFF | decreasing | - | - | increasing |
| Mode 2 | OFF | ON | increasing | decreasing | increasing | decreasing |
| Mode 3 | ON | OFF | increasing | decreasing | decreasing | increasing |
| Mode 4 | ON | ON | - | increasing | - | decreasing |

Table 1 Output and FC voltage states

The transfer function (y) of the Flying Capacitor booster is the following:

$$y = \frac{V_{OUT}}{V_{IN}} = \frac{1}{1-D}$$

Where D is the duty cycle.

The used modes are depending on the duty cycle. If $D < 0.5$ than $y < 2$. In this case Mode 4 is not used and the operation will be the following:

... → Mode 1 → Mode 2 → Mode 1 → Mode 3 → ...

If $D > 0.5$ than $y > 2$ and the operation will be:

... → Mode 4 → Mode 2 → Mode 4 → Mode3 → ...

In case of $D = 0.5$, $y = 2$ the operation:

... → Mode 2 → Mode 3 → Mode 2 → Mode3 → ...

The most commonly used operation when D is less than 0.5.

2.2 The operation of the Flying Capacitor Booster

In the flying capacitor booster topology the two transistor have to be controlled by 180° phase shifting (Figure 4).


 


Figure 4 The reference and modulation signals for the PWM

This results that in case of $D = 0.5$, the operation modes will change between Mode 2 and Mode 3. The typical curves of the flying capacitor booster can be seen on Figure 5 in case of $D = 0.2$.

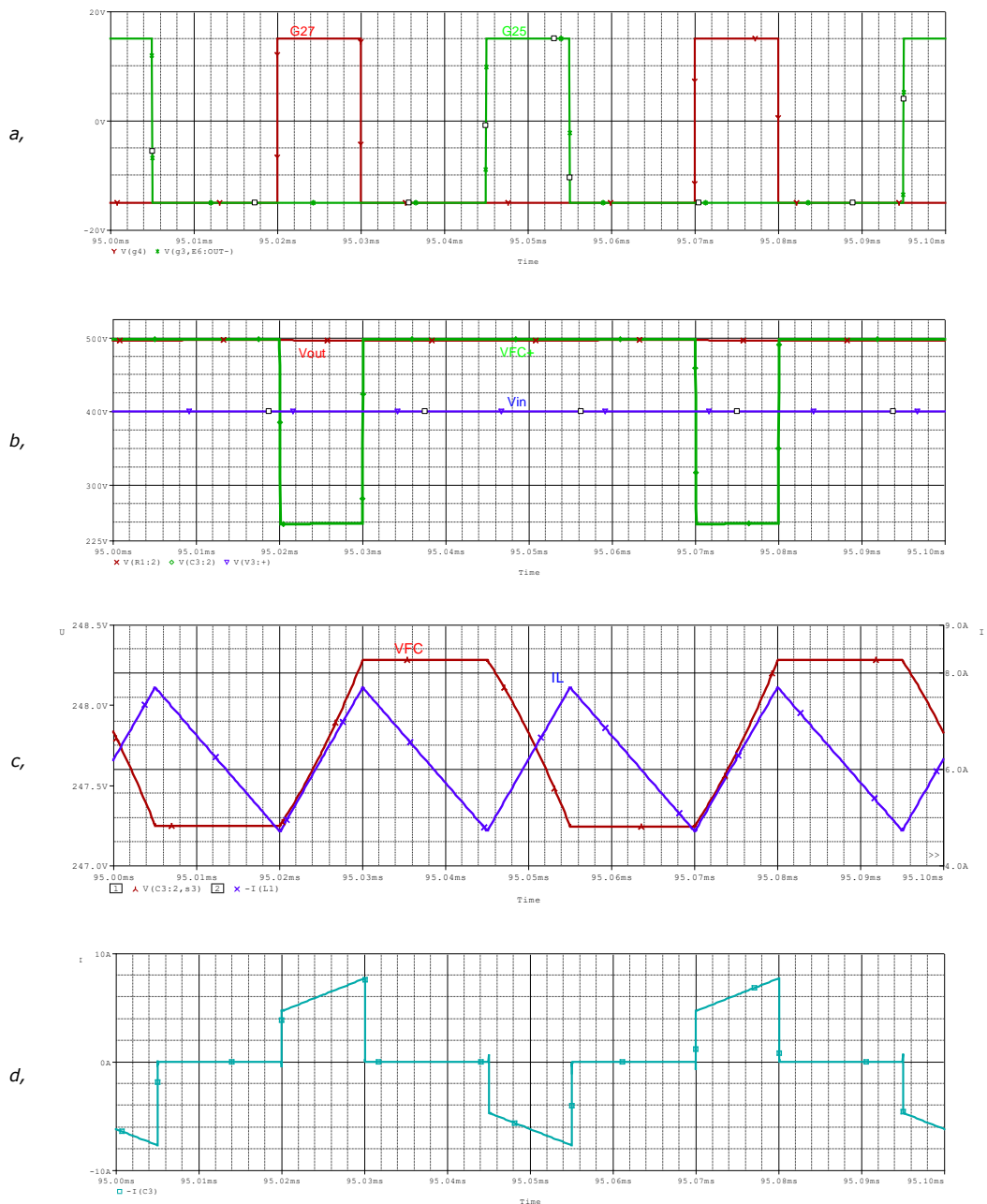

 


Figure 5 The typical curves:

- a, the gate signals*
- b, the output, the input and the FC+ voltage*
- c, the voltage of the Flying Capacitor and the inductor current*
- d, the Flying Capacitor current*
- e, the currents of the diodes*
- f, the current of the transistors*

2.3 The advantages of the Flying Capacitor Booster

The Flying Capacitor Booster topology compared to the booster topology has the following advantages:

- As the operation is three level, the voltage stress on the semiconductor will be decreased. This resulting lower EMI, lower current and voltage ripple.

The Flying Capacitor Booster topology compared to the symmetrical booster topology has the following advantages:

- It has two level input and output connection, while the third voltage level is synthesized by the flying capacitor. This way the large three level capacitors can be eliminated on the input and the output.
- Only one input choke is needed.

In both cases the input frequency is double of the switching frequency. This results a lower input ripple current or the inductance can be decreased. Because of the double frequency slower semiconductors can be used, what is decreasing the cost while the switching losses will be also lower. This means for optimal behavior SiC MOSFETs are not needed, Si IGBTs can be used.

For more detailed comparison of the topologies and component selection please see Vincotech's benchmark "Boost your 1500 V string inverter" [1].

3 The Flying Capacitor

3.1 Sizing of the Flying Capacitor

The voltage supplied by the flying capacitor has a key role in this topology. To keep the voltage ripple on the capacitor low suitable capacitor size is needed. To determine the needed capacitance the switching frequency and the maximum allowed voltage ripple need to be considered. The size of the capacitance can be calculated as:

$$C_{FC} = \frac{I_{peak}}{\Delta U_{FC} \cdot 2f_{SW}}$$

, where ΔU_{FC} is the maximum allowed voltage ripple, I_{peak} is the maximum current, f_{SW} is the switching frequency of the transistors.

3.2 The balancing of the capacitor voltage

For the appropriate operation the Flying Capacitor voltage has to be half of the output voltage. To achieve this, it must be regulated at all time. This can be done by changing the operation modes. As it can be seen in Table 1 Mode 1 and Mode 4 has no effect for the Flying Capacitor, so for regulation Mode 2 and Mode 3 have to be used. The regulation state diagram can be seen on Figure 6.

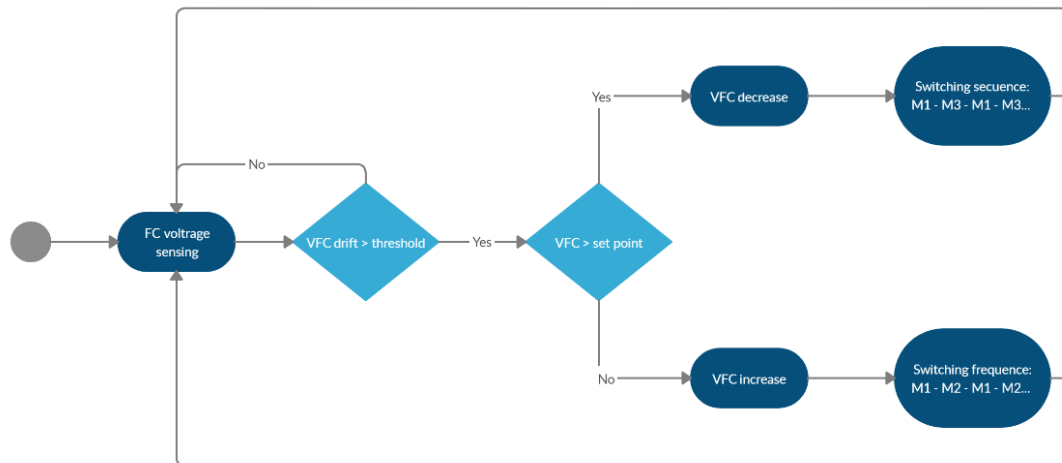


Figure 6 The Flying Capacitor regulation

As it was mentioned previously, the needed modes are depending on the duty cycle. In case of $D \leq 0.5$ the operation will be the following:

... → Mode 1 → Mode 2 → Mode 1 → Mode 3 → ...

If the Flying Capacitor voltage exceeds the set point the operation can be modified to decrease the voltage:

... → Mode 1 → Mode 3 → Mode 1 → Mode 3 → ...

If the Flying Capacitor voltage is less than the set point:

... → Mode 1 → Mode 2 → Mode 1 → Mode 2 → ...

In case of $D \geq 0.5$ the needed modification will be the same only Mode 4 will be used instead of Mode 1:

... → Mode 4 → Mode 3 → Mode 4 → Mode 3 → ... to decrease the voltage

... → Mode 4 → Mode 2 → Mode 4 → Mode 2 → ... to increase the voltage

3.3 The pre-charge of the capacitor [2]

This section will describe the details of the method proposed by Mitsubishi Electric Corporation to protect the flying capacitor booster when there aren't control signals (e.g.: during startup). This method is protected by DC/DC POWER CONVERSION APPARATUS[®] patent of the United States Patent Office. See section 3.3.2 on page 17 for further information on the applicable patent family and the option for sublicensing.

In case when all the control signals of the transistors are low, the flying capacitor voltage can't be regulated. In that operation extra effort needed to keep the flying capacitor voltage on the safe side to eliminate the overvoltage on the semiconductors which will cause a fatal error in the system. There are two operation modes when all the transistors are OFF. When the input is applied and the output is equal with the input (e.g.: startup). And when the input is zero and the output is not. This happens for example when one string is not connected to the circuit and other boosters are working. In all the two cases the voltage of the flying capacitor is zero, and the voltage sharing of the two transistors is not defined. To keep the voltage level of the semiconductors below the breakdown voltage additional balancing have to be used.

During startup the current will flow thru the two diodes and charge the output capacitance. In this case the output voltage will be equal to the input voltage while the flying capacitor voltage is zero. This is dangerous for the lower switch. To eliminate this problem another current path have to be added, where the current will be able to charge the flying capacitor also. For this a diode can be used which cathode have to be connected to a capacitive voltage divider, where the lower point of the flying capacitor is clamped at the half of the DC-link voltage. This can be seen on Figure 7.

 


Figure 7 The additional current path during startup

As the voltage of the capacitor can be calculated from the following expression: $V = \frac{Q}{C}$, and the charge will be the same for C_{out1} and $C_{out2} + C_{FC}$, the flying capacitor voltage will be the following:

$$V_{FC} = V_{OUT} \frac{C_{out1}}{C_{out1} + C_{out2} + C_{FC}}$$

, where V_{OUT} is equal with V_{In} (if the forward voltage of the diodes is not considered).

If the capacitance of C_{out1} and C_{out2} is equal and the capacitance of C_{FC} is significantly smaller than the capacitance of C_{out1} and C_{out2} , the voltage of the flying capacitor is half of the output.

$$C = C_{out1} = C_{out2}, \quad C_{FC} \ll C, \quad V_{FC} \approx \frac{V_{In}}{2}$$

When the string is not used and other boosters are working, the input voltage is zero, while the output voltage is not. In this case another diode has to be added to charge the flying capacitor.

 


Figure 8 The additional diode when V_{in} is zero

As it can be seen on Figure 8 the current path will be the following:

$$C_{out2} \rightarrow Dh \rightarrow C_{FC} \rightarrow D45 \rightarrow L \rightarrow C_{in}$$

In this case the sum of the flying capacitor voltage and the input voltage can be calculated as the following:

$$V_{fci} = V_{OUT} \frac{C_{out2}}{C_{out1} + C_{out2} + C_{FC} \times C_{in}}$$

As in the last expression, if C_{out1} and C_{out2} is equal and $C_{FC} \times C_{in}$ is negligible compared to C_{out1} and C_{out2} the voltage is half of the output voltage.

$$C = C_{out1} = C_{out2}, \quad C_{FC} \times C_{in} \ll C, \quad V_{fci} \approx \frac{V_{OUT}}{2}$$

This voltage will be divided on the two capacitors. If the capacitance of the C_{FC} is much smaller than the C_{in} capacitor then the voltage of the C_{in} capacitor is as low as it can be considered zero and the voltage of the flying capacitor is near to the half of the output voltage.

This method can be improved by closing T27 switch. In this case the voltage is not divided by C_{in} and C_{FC} capacitors and the current path will be the following:

$$C_{out2} \rightarrow Dh \rightarrow C_{FC} \rightarrow T27$$

And the flying capacitor voltage:

$$V_{FC} = V_{OUT} \frac{C_{out2}}{C_{out1} + C_{out2} + C_{FC}}$$

3.3.1 Design considerations

During normal operation T27 will create an overvoltage spike at turn-off. If Df turns on to clamp this spike T27 switch will be loaded with the reverse recovery of Df. To avoid Df clamping this overvoltage spike an additional Zener diode (Dz) can be added in series with Df. The Zener voltage of the Zener diode should be higher than the spike of turn-off. This can be seen on Figure 9.

 


Figure 9 The additional Zener diode

If the voltage of flying capacitor is extremely higher than $\frac{V_{OUT}}{2}$ an additional current ripple will appear on the inductor. This ripple causes increased losses and noise. This ripple can be also moderated with this Zener diode.

If the voltage of C_{FC} is less than the voltage of C_{out2} an equalization current will flow between C_{FC} and C_{out2} resulting an unbalance between C_{out1} and C_{out2} . This unbalance can be decreased with a current limiting resistor (R_f) which can be seen on Figure 10.

 


Figure 10 The current limiting resistor

3.3.2 Patent sublicensing

Mitsubishi Electric Cooperation holds the Japanese patent and all related patents in the patent family of JP 5379248 covering the flying capacitor pre-charge procedures described above. Vincotech is a group company of Mitsubishi Electric Corporation and eligible to sublicense the aforementioned patent. The sublicensing agreement is bound to the usage of Vincotech power modules and allows the customer to use the patent without royalties.

To get further information about the sublicensing process and conditions please directly contact your local sales person or use the contact form on www.vincotech.com

4 Conclusion

The flying capacitor booster is a highly efficient low-cost solution for solar inverter applications. The main advantages are the frequency multiplication, the lower semiconductor voltage, the lower voltage and current ripple, the lower switching losses and the low EMI emission. The challenge is to regulate the voltage of the flying capacitor when all the transistors are in OFF state. This challenge can be solved easily by additional diodes based on Mitsubishi Electric Corporation's patent. With these diodes the flying capacitor booster is a cost-efficient alternative for the other booster solutions with higher efficiency.

5 References

- [1] M. Tauer, "Boost your 1500 V string inverter," Unterhaching.
- [2] T. Okuda and H. Ito, "DC/DC POWER CONVERSION APPARATUS". United States Patent US 2013/0021011 A1, 24 01 2013.