



Vincotech

# **dV/dT VALIDATION IN MOTOR DRIVES**

EMPOWERING YOUR IDEAS



## Table of Contents

1	Why dV/dt validation is important.....	1
2	What edge steepness depends on .....	1
3	How dV/dt is determined .....	2
4	Assessment of the measurement result .....	3
5	Edges / IGBT assignment .....	6
6	How the quality of the measurement can be improved .....	9
7	Choosing a reasonable sampling time.....	13
8	Accuracy, limitations and features of this method .....	14
9	Summary .....	14

**Published in Bodo's Power System magazine in March 2025**



# **dV/dt validation in motor drives**

*Marcus Preuß, Field Application Engineer EMEA, Vincotech*

dV/dt validation in motor drives – how the edge steepness of an inverter can be quickly and practically tested with the oscilloscope without having to manually assess each individual edge in the time domain. A method that can be applied both during the development process in the lab as well as directly on the end application with the final customer in the field.

## **1 Why dV/dt validation is important**

If the edge steepness of the voltage of a motor phase – hereinafter dV/dt – is too high, it can cause damage to the windings through partial discharge in the motor windings. A limit value widely used in the industry is 5 kV/μs. Limit values must be adhered to and checked to protect motors. While this is often performed during the development process with double pulse tests in the lab, this article focuses on the testing of the end application under real operating conditions.

It is important to understand that there are many different edges within a phase current period. At 50 Hz phase current and 2 kHz switching frequency, there are 80 different edges, including 40 positive and 40 negative. At 16 kHz there are already 640 edges to be assessed for each load condition. Consequently, there is a need for a rapid measurement method, because the manual assessment of each individual edge in the time domain is too time-consuming.


## **2 What edge steepness depends on**

The steepness of the edges and their distribution within the phase current period primarily depends on the power semiconductors and their gate resistors. Additional secondary influencing factors include: motor load, transient processes during the dead time (soft switching), phase current direction, phase current amplitude, power factor, type of PWM (pulse width modulation), diode snappiness, type and length of the cable, temperature of the semiconductors and the layout of the circuit board and power module.

### 3 How dV/dt is determined

The following two parameters are recorded with an oscilloscope:

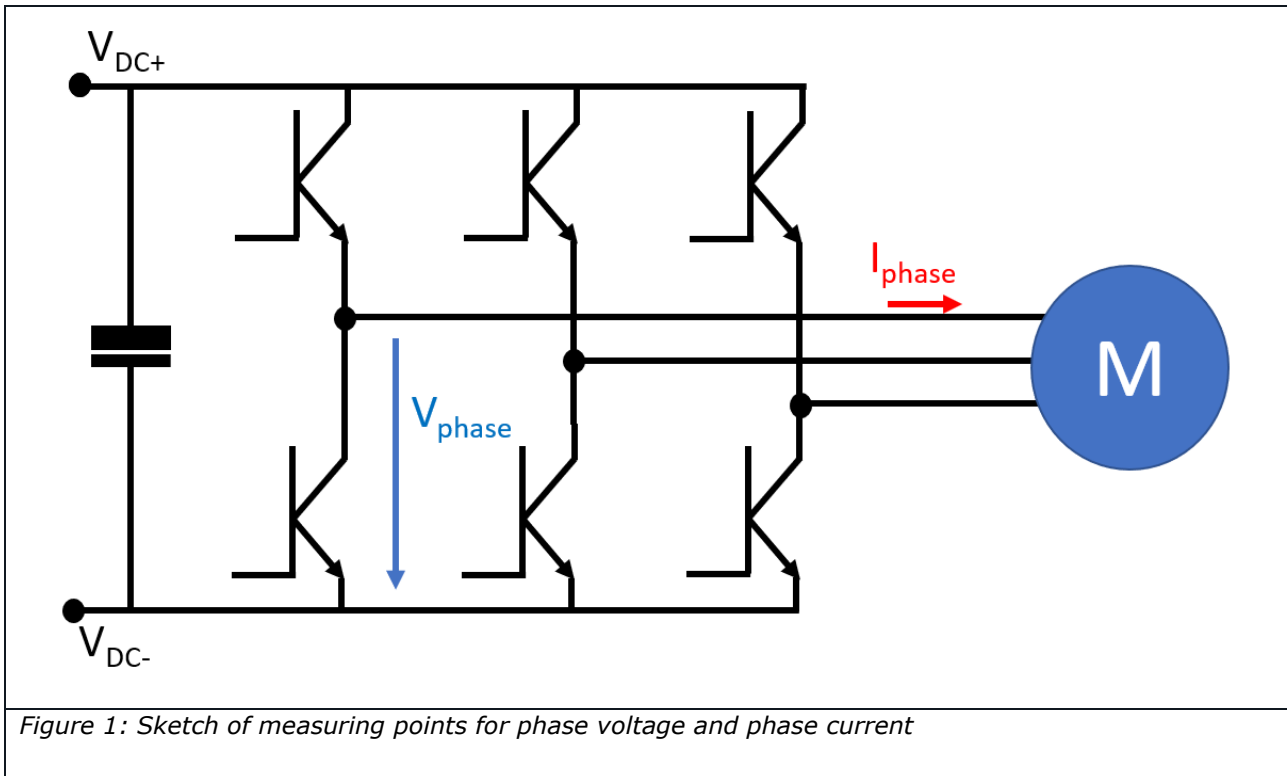- a) phase current
- b) switched phase voltage



The switched phase voltage is now differentiated and scaled with the help of a math channel of the oscilloscope. The differentiation transforms the edge steepness from the time domain to the amplitude domain. The scaling standardizes the result to kV/μs.

The transformation into the amplitude domain has the advantage that the result can be directly read on the y-axis. Thus, the laborious assessment of each edge in the time domain is no longer necessary.

**Formula for the math channel:**

$$\frac{kV}{\mu s} = \text{derivative (Phasenspannung)} \times 10^{-9}s$$

It is useful to select the measuring period so that exactly one complete period of the phase current is displayed on the oscilloscope. This means that all edges of a specific operating state can be recorded and mapped in a single shot.

## 4 Assessment of the measurement result

The  $dV/dt$  can be read directly from the math channel. It can be seen at a glance whether all edges of a period are within the set limit or whether limit values have been exceeded (green spikes in the figure 2).

 


Figure 2:  $dV/dt$  measurement

(2.2 kW three-phase asynchronous motor, no-load)

Ch1=Phase voltage against DC-  
 Ch2= Phase current  
 MC=  $dV/dt$

### Properties

Sample interval	8 ns
Sample rate	125 MS/s
No. samples	2,500,000
Hardware Resolution	15 bits

If a limit value of 5 kV/ $\mu$ s had been taken as the reference in the above example, it would be immediately seen that this limit value had been significantly exceeded except in the zero-crossing area of the phase current.



Figures 3 and 4 show the close-up shots of an (a) falling and (b) rising edge. You can clearly see how the  $dV/dt$  calculation maps the real edge.

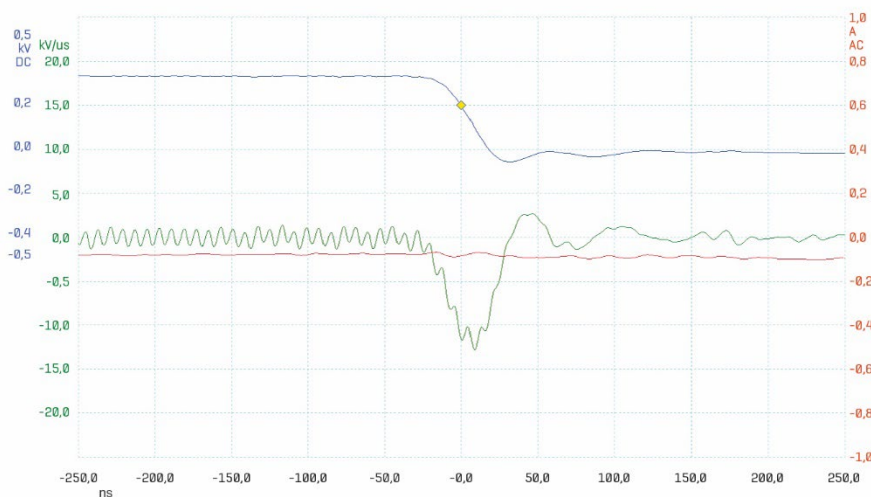


Figure 3: Falling edge (detail view)  
(90 W three-phase asynchronous motor, no-load)

Ch1=Phase voltage against DC-  
Ch2= Phase current  
MC=  $dV/dt$

Properties

Sample interval	8 ns
Sample rate	125 MS/s
No. samples	63
Hardware Resolution	14 bits

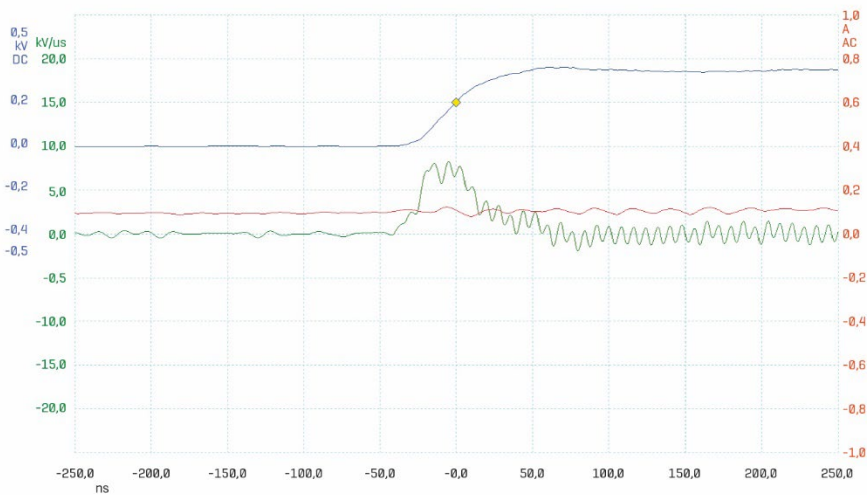


Figure 4: Rising edge (detail view)  
(90 W three-phase asynchronous motor, no-load)

**Ch1=Phase voltage against DC-**  
**Ch2= Phase current**  
**MC=  $dV/dt$**

**Properties**

Sample interval	8 ns
Sample rate	125 MS/s
No. samples	63 (670)
Hardware Resolution	14 bits

## 5 Edges / IGBT assignment

If the edge steepness is too high, it must be optimized. In the simplest case, the gate resistors can be adjusted. For optimization, every edge that is too steep must be assigned to the responsible IGBT (insulated-gate bipolar transistor) and its switching direction. In simple terms: You have to know whether the HS (high side) or LS (low side) IGBT is responsible and whether it is currently turning on or off. The assignment requires a case differentiation for (a) the direction of the phase current and (b) the direction of the  $dV/dt$ .

The following table lists the correct assignment:


Current direction	$dV/dt$	Responsible IGBT	Equivalent circuit diagram
positive →	positive ↑	HS IGBT (turn on)	
positive →	negative ↓	HS IGBT (turn off)	
negative ←	positive ↑	LS IGBT (turn off)	
negative ←	negative ↓	LS IGBT (turn on)	

HS = high Side; LS = low side

*Table 1: Assignment table of the responsible IGBT to the edge*



Figure 5 illustrates the content of the above table in graphical form.

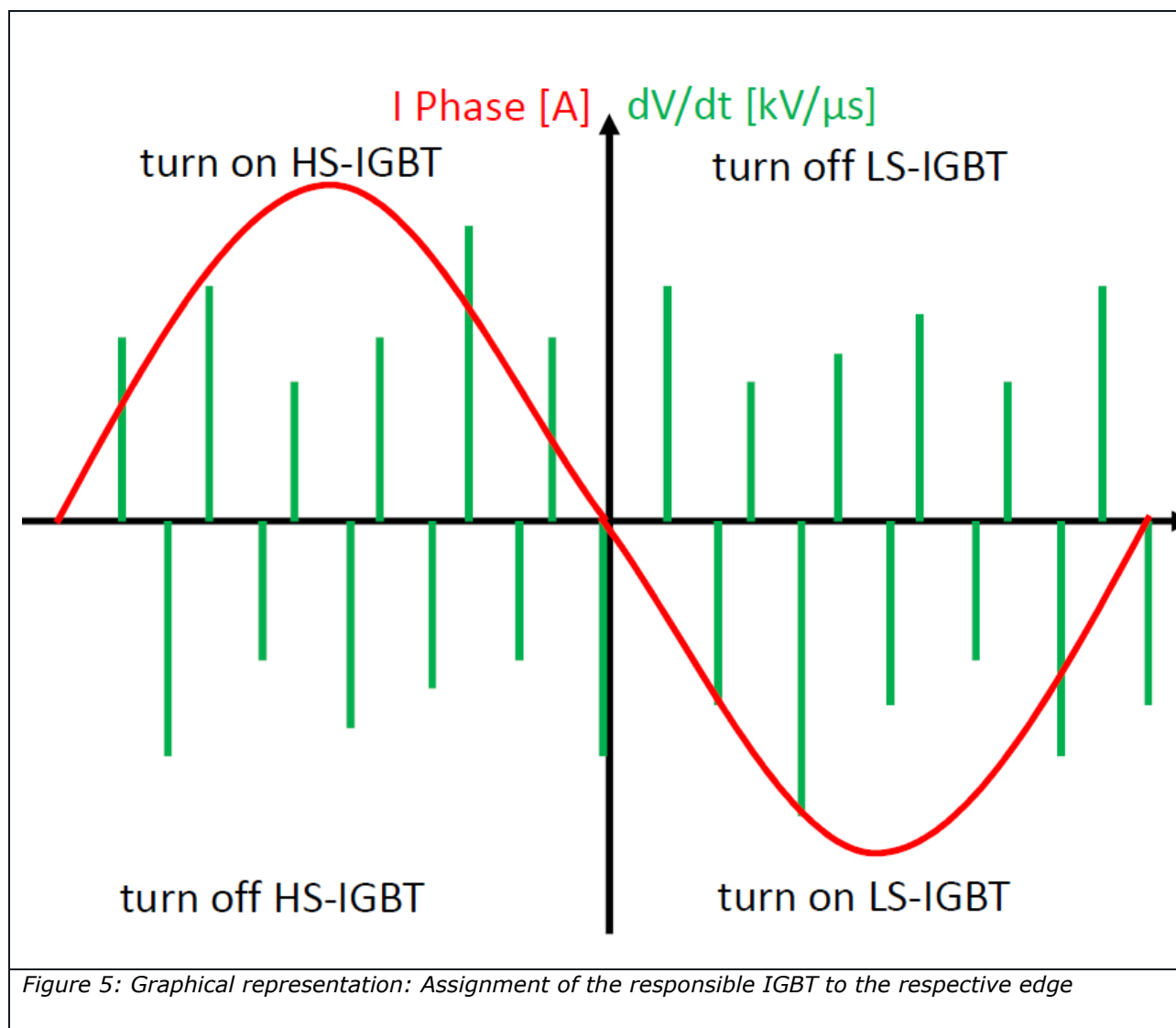

A practical example is given below. Figure 6 illustrates the assignment of the IGBTs of a flat-top PWM switched inverter.

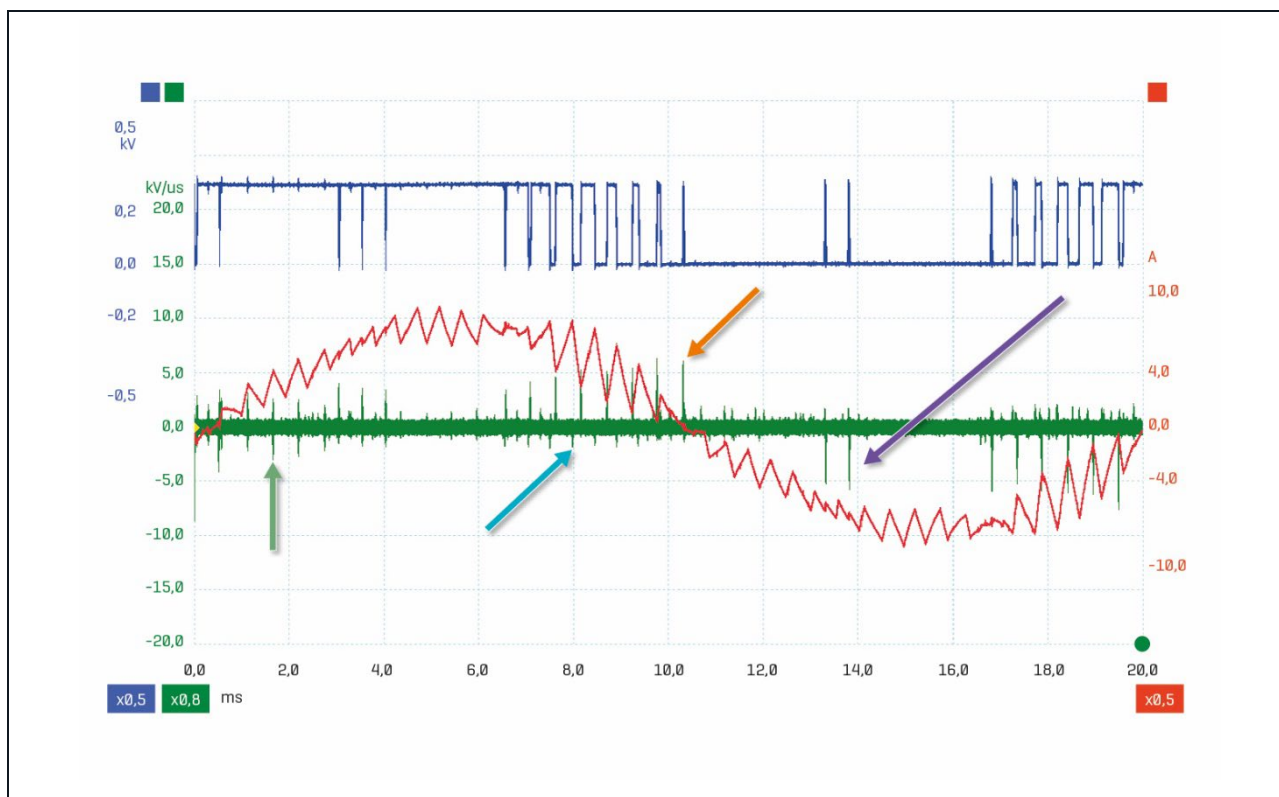


Figure 6:  $dV/dt$  measurement  
(2.2 kW three-phase asynchronous motor, flat-top PWM, load)

Ch1=Phase voltage against DC-  
Ch2= Phase current  
MC=  $dV/dt$

Properties	
Sample interval	8 ns
Sample rate	125 MS/s
No. samples	2,500,000
Hardware Resolution	15 bits

**Orange arrow:**  $dV/dt = \text{positive}$  & phase current = positive => Turn on HS IGBT

**Violet arrow:**  $dV/dt = \text{negative}$  & phase current = negative => Turn on LS IGBT

**Turquoise arrow:**  $dV/dt = \text{negative}$  & phase current = positive => Turn off HS IGBT

**Green arrow:** No edge; i.e. it is a step edged capacitive coupling from the neighboring phase.

Note: With fast edges and high capacitive coupling between the motor phases, crosstalk phenomena occur. These are made visible through step pulses on the phase voltage and consequently are also evaluated by the method presented here. However, this is not critical because for physical reasons, the crosstalk phenomena cannot be steeper than the edges



themselves. If in doubt, zooming into the measurement will provide information as to whether it is an edge or a crosstalk phenomena.

**Additional information: Notes on the equivalent circuit diagrams in Table 1**

Drawing an equivalent circuit diagram for the half bridge of a phase can simplify the explanation of the commutation behavior, because every equivalent circuit diagram contains only one active IGBT. The half bridge of a phase operates as a BUCK stage if the phase current is positive, and as a BOOST stage if the phase current is negative. The half bridge of a phase can therefore be broken down into two equivalent circuit diagrams, namely into an **(a) buck stage** and **(b) boost stage**. In doing so, the diode simulates the anti-parallel diode of the opposite IGBT, which is always conductive during the dead time. (Precondition: non-gap operation, which is almost always present in inverter operation).

## 6 How the quality of the measurement can be improved


A number of obstacles must be overcome to achieve a good result because the quality and accuracy of the calculated  $dV/dt$  very much depends on the noise of the math channel. It occurs during the calculation and is not signal noise!

**Note:** The accuracy of the calculated  $dV/dt$  is heavily dependent on the noise.

$$\text{calculated } dV/dt = \frac{dV + \text{Noise}}{dt}$$

For a proper result, the noise must be significantly smaller than the  $dV/dt$  of the switching edges (signal-to-noise ratio).

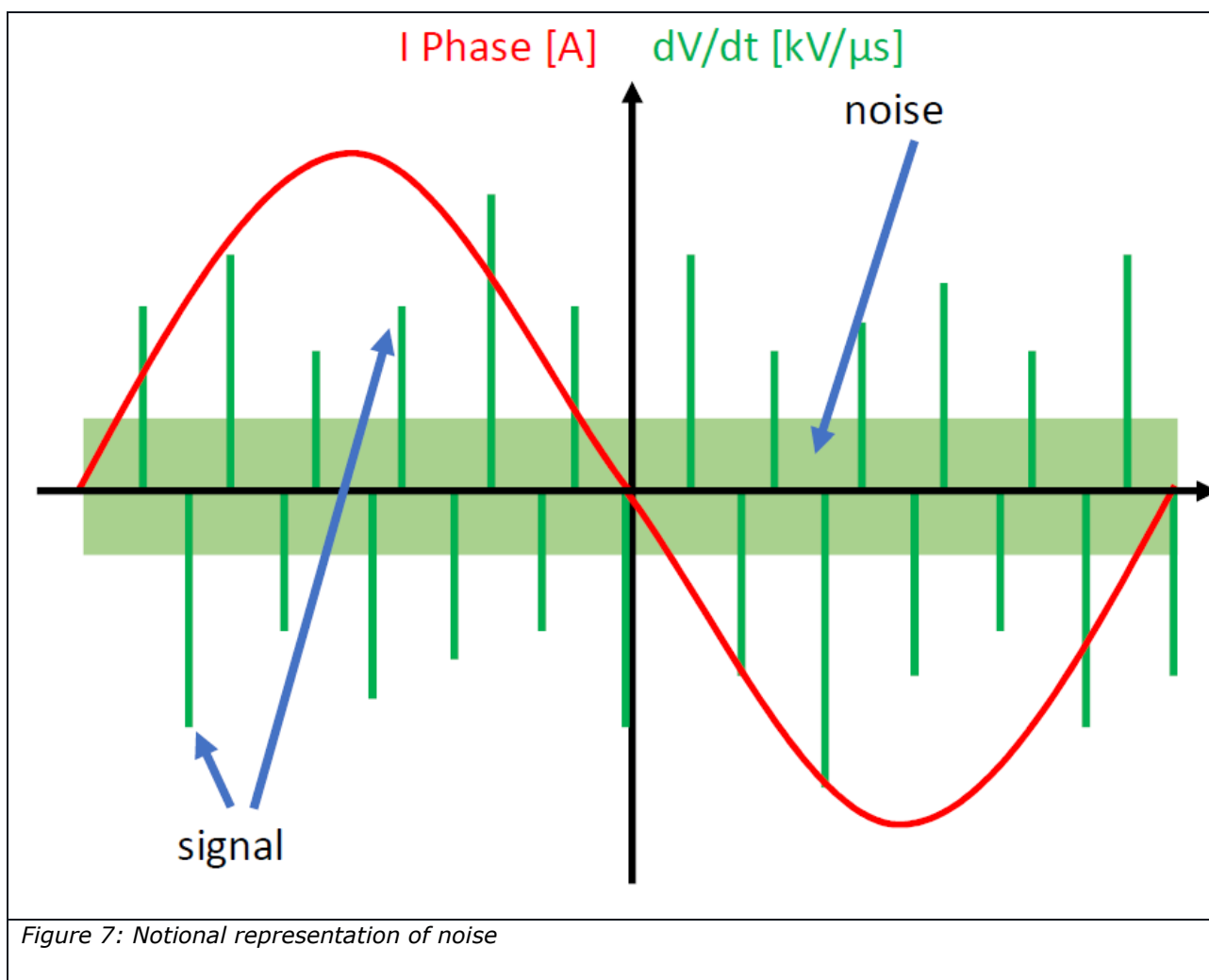It is therefore important to know where the noise is coming from and how it can be kept to a minimum.



**Note:** Noise can be reduced by (a) higher vertical AD resolution, (b) the smallest possible measuring range and (c) a lower sampling rate.

The following comparison illustrates how a higher AD resolution and a longer sampling time reduce noise. The following measurement settings are compared:

- a) 15-Bit AD resolution / 8 ns sampling time (Fig. 8)
- b) 8-Bit AD resolution / 2 ns sampling time (Fig. 9)



Fig. 8 shows that a **high** AD resolution (15-bit) and a **long** sampling time (8 ns) result in **low** noise.

 


Figure 8: Low noise with 15-bit / 8 ns

Ch1=Phase voltage against DC-  
Ch2 = Phase current (filtered)  
MC= dV/dt

Properties	
Sample interval	8 ns
Sample rate	125 MS/s
No. samples	2,500,000
Hardware Resolution	15 bits



Fig. 9 shows that a **low** AD resolution (8-bit) and a **short** sampling time (2 ns) result in **high** noise.

 


Figure 9: High noise with 8-bit / 2 ns

Ch1=Phase voltage against DC-  
Ch2 = Phase current (filtered)  
MC= dV/dt

Properties

Sample interval	2 ns
Sample rate	500 MS/s
No. samples	9,968,003
Hardware Resolution	8 bits

The difference in noise is clearly visible. In Fig. 9 the noise is even higher than a frequently used limit value ( $> 5\text{kV}/\mu\text{s}$ ) and would thus be unusable for this limit value measurement.

**Additional information: Where does the noise in the math channel come from?**

The cause is essentially the quantization noise of the oscilloscope's AD converter. It causes a high-frequency amplitude error. It results in a  $dV/dt$  error during the differentiation in the math channel. The noise in the math channel is the sequence of all  $dV/dt$  errors and becomes larger the greater the quantization error (AD resolution and measuring range) and the shorter the sampling time. (Sampling rate)

## 7 Choosing a reasonable sampling time

Noise increases and the quality of the result decreases as the sampling rate increases.

It is therefore necessary to select a reasonable sampling time. The sampling time must be (a) long enough to keep the noise sufficiently low and (b) short enough to ensure that the edges are sampled with sufficient resolution.

A good compromise is to choose a sampling time that creates about 3 measurement segments (4 samples) within an edge.

For example, the sampling rate should be about 8 ns for a 32 ns edge time (80% / 20%).

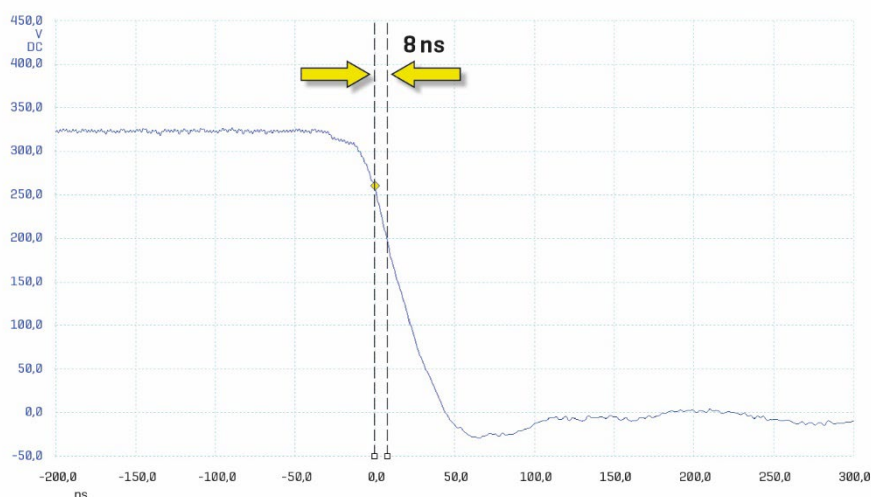


Figure 10: Edge length v. sampling time

Ch1=Phase voltage

### Properties

Sample interval	2 ns
Sample rate	500 MS/s
No. samples	250 (2540)
Hardware Resolution	12 bits

This is illustrated in Fig. 10. The time between the cursors corresponds to 8 ns and is therefore equal to the sensible sampling time. Three different sections are measured within the edge. The edge is sufficiently well sampled. This is a good compromise between sampling time and noise and results in a good signal-to-noise ratio.



## 8 Accuracy, limitations and features of this method

Of course, this method has its limitations. The calculated edge steepness is always the average value between two measuring points. If there is a steeper section between these points, it will not be detected. However, experiments have shown that good results for a practical, non-scientific assessment can be achieved. This method is less suitable for scientific requirements in which even the smallest partial sections of an edge must be assessed. In this case, every single edge must be sampled with the maximum possible sampling rate and be laboriously assessed in the time domain.

## 9 Summary

It has been shown that forming the derivative of the phase voltage is a really quick, simple and practical way to assess the edge steepness on the motor drive.

It is important to select a reasonable sampling rate, a good vertical resolution and the smallest possible measuring range.

### About the author



Marcus Preuß is a Field Application Engineer for Vincotech in Unterhaching, Germany. He advises Vincotech's major customers on the selection of power modules and provides them with the necessary application support during the development process. Vincotech's extensive portfolio covers many topologies, primarily for the markets for industrial drives, solar inverters and battery charging. Marcus has many years' experience in power electronics, analog and mixed signal circuit design including field support and troubleshooting.

# Vincotech GmbH

Biberger Strasse 93

82008 Unterhaching / Germany

T +49 89 878 067-0 / F +49 89 878 067-300

[www.vincotech.com](http://www.vincotech.com)